

Alexander & Sadiku Practice Problem 10.1
Michael Gustafson

> restart

Handy functions for dealing with phasors

> $j := I$:

> $polard := (mag, angd) \rightarrow polar(mag, angd * \pi / 180)$:

> $argumentd := (num) \rightarrow argument(num) * 180 / \pi$:

> $listphasors := \text{proc}(plist) \text{ local } k$
for k **from** 1 **to** $nops(plist[])$ **do**
 $printf("%s = \%f < \%f \text{ deg}\backslash n", lhs(plist[][k]), evalc(abs(rhs(plist[][k]))),$
 $evalc(argumentd(rhs(plist[][k])))$)
end do end proc:

Circuit equations

> $KCLn1 := -I_a + \frac{(V1 - 0)}{R1} + (V1 - V2) \cdot j\omega C = 0$:

> $KCLn2 := (V2 - V1) \cdot j\omega C + \frac{(V2 - 0)}{j\omega L} + \frac{(V2 - b \cdot Vx)}{R2} = 0$:

> $CTRL := Vx = V1$:

Solve circuit equations

> $MySoln := solve(\{KCLn1, KCLn2, CTRL\}, [V1, V2, Vx])$:

Collect $j\omega$ to put into more useful form

> $collect(MySoln, j\omega)$

$$\left[\left[\begin{aligned} V1 &= -\frac{I_a R1 (C L R2 j\omega^2 + L j\omega + R2)}{(C L R1 b - C L R1 - C L R2) j\omega^2 + (-C R1 R2 - L) j\omega - R2}, V2 \\ &= -\frac{I_a R1 L j\omega (C R2 j\omega + b)}{(C L R1 b - C L R1 - C L R2) j\omega^2 + (-C R1 R2 - L) j\omega - R2}, Vx \\ &= -\frac{I_a R1 (C L R2 j\omega^2 + L j\omega + R2)}{(C L R1 b - C L R1 - C L R2) j\omega^2 + (-C R1 R2 - L) j\omega - R2} \end{aligned} \right] \right] \quad (1)$$

Define lists for known values

> $Vals := R1 = 2, R2 = 4, L = 2, C = 0.2, j\omega = j \cdot 2, I_a = polard(10, 0), b = 3$:

Find numerical solutions

> $MySoln := subs(Vals, MySoln)$:

Find phasors

> $listphasors(MySoln)$

$V1 = 11.327042 < 60.018361 \text{ deg}$

$V2 = 33.023719 < 57.127091 \text{ deg}$

$Vx = 11.327042 < 60.018361 \text{ deg}$

>

Conclusion: $v1(t) = vx(t) = 11.327 \cos(2 t + 60.01 \text{ deg})$, $v2(t) = 33.024 \cos(2 t + 57.13 \text{ deg})$