

Alexander & Sadiku Example Problem 10.6
 Michael Gustafson

> restart

Handy functions for dealing with phasors

> $j := I$

$$j := I \quad (1)$$

> $polard := (mag, angd) \rightarrow polar(mag, angd * Pi / 180)$

$$polard := (mag, angd) \rightarrow polar\left(mag, \frac{1}{180} angd \pi\right) \quad (2)$$

> $argumentd := (num) \rightarrow argument(num) * 180 / Pi$

$$argumentd := num \rightarrow \frac{180 argument(num)}{\pi} \quad (3)$$

> **listphasors := proc (plist) local k**
for k from 1 to nops(plist[]) do
 printf("%s = %f < %f deg\n", lhs(plist[][k]), evalc(abs(rhs(plist[][k]))),
 evalc(argumentd(rhs(plist[][k]))))
end do end proc:

Circuit equations

> $KCLn2 := \frac{(Vn2 - Va)}{j \cdot \omega \cdot L} - Ib + \frac{Vo}{R1} = 0$

$$KCLn2 := -\frac{I(Vn2 - Va)}{\omega L} - Ib + \frac{Vo}{R1} = 0 \quad (4)$$

> $KCLn3 := -\frac{Vo}{R1} + j \cdot \omega \cdot C \cdot (Vn2 - Vo) + \frac{(Vn2 - Vo - Vc)}{R2} = 0$

$$KCLn3 := -\frac{Vo}{R1} + I \omega C (Vn2 - Vo) + \frac{Vn2 - Vo - Vc}{R2} = 0 \quad (5)$$

Solve circuit equations

> $MySoln := solve(\{KCLn2, KCLn3\}, [Vn2, Vo])$

$$MySoln := \left[\left[\begin{aligned} Vn2 = & -\left(I \left(\omega L Vc - I Va R2 + \omega C R1 R2 Va - I R1 Va + Ib \omega L R2 \right. \right. \right. \\ & \left. \left. \left. + I \omega^2 C R1 R2 Ib L + Ib \omega L R1 \right) \right) / \left(-I \omega L + \omega^2 L C R2 - R2 - I \omega C R1 R2 \right. \right. \\ & \left. \left. - R1 \right), Vo = \frac{R1 \left(Vc - Va - I Ib \omega L - I \omega C R2 Va + \omega^2 C R2 Ib L \right)}{-I \omega L + \omega^2 L C R2 - R2 - I \omega C R1 R2 - R1} \right] \right] \quad (6) \end{aligned}$$

Define lists for each frequency independently

> $Valsa := R1 = 1, R2 = 4, L = 2, C = 0.1, \omega = 2, Va = polard(10, 0), Ib = 0, Vc = 0$
 $Valsa := R1 = 1, R2 = 4, L = 2, C = 0.1, \omega = 2, Va = polar(10, 0), Ib = 0, Vc = 0 \quad (7)$

> $Valsb := R1 = 1, R2 = 4, L = 2, C = 0.1, \omega = 5, Va = 0, Ib = polard(2, -90), Vc = 0$

$Valsb := R1 = 1, R2 = 4, L = 2, C = 0.1, \omega = 5, Va = 0, Ib = polar\left(2, -\frac{1}{2} \pi\right), Vc = 0 \quad (8)$

> $V_{alsc} := R1 = 1, R2 = 4, L = 2, C = 0.1, \omega = 0, V_a = 0, I_b = 0, V_c = \text{polar}(5, 0)$
 $V_{alsc} := R1 = 1, R2 = 4, L = 2, C = 0.1, \omega = 0, V_a = 0, I_b = 0, V_c = \text{polar}(5, 0)$ (9)

Find solutions for each frequency

> $MySolna := \text{subs}(Valsa, MySoln)$
 $MySolna := [[Vn2 = (0.1826484018 + 0.06849315068 I) (-5 I \text{polar}(10, 0) + 0.8 \text{polar}(10, 0)), Vo = (-0.06849315068 + 0.1826484018 I) (-\text{polar}(10, 0) - 0.8 I \text{polar}(10, 0))]]$ (10)

> $MySolnb := \text{subs}(Valsb, MySoln)$
 $MySolnb := \left[\left[Vn2 = (0.03252032520 - 0.04065040650 I) \left(50 \text{polar}\left(2, -\frac{1}{2} \pi\right) + 20.0 I \text{polar}\left(2, -\frac{1}{2} \pi\right) \right), Vo = (0.04065040650 + 0.03252032520 I) \left(-10 I \text{polar}\left(2, -\frac{1}{2} \pi\right) + 20.0 \text{polar}\left(2, -\frac{1}{2} \pi\right) \right) \right] \right]$ (11)

> $MySolnc := \text{subs}(Valsc, MySoln)$
 $MySolnc := [[Vn2 = 0. - 0. I, Vo = (-0.2000000000 + 0. I) \text{polar}(5, 0)]]$ (12)

Find phasors for each frequency

> $\text{listphasors}(MySolna)$
 $Vn2 = 9.877484 < -60.353678 \text{ deg}$
 $Vo = 2.498097 < -30.784147 \text{ deg}$

> $\text{listphasors}(MySolnb)$
 $Vn2 = 5.606810 < -119.538782 \text{ deg}$
 $Vo = 2.328101 < -77.905243 \text{ deg}$

> $\text{listphasors}(MySolnc)$
 $Vn2 = 0.000000 < \text{NaN deg}$
 $Vo = 1.000000 < 180.000000 \text{ deg}$

Conclusion: $v_o(t) = 2.498 \cos(2 t - 30.78 \text{ deg}) + 2.328 \cos(5 t - 77.91 \text{ deg}) - 1$
 $v_o(t) = 2.498 \cos(-2 t + 30.78 \text{ deg}) + 2.328 \cos(-5 t + 77.91 \text{ deg}) - 1$ (13)

>